

# High Performance CMOS Radio Design for Multi Band OFDM UWB

Nathan R. Belk  
August 22, 2004

1

## Acknowledgements

We would like to thank the authors of Texas Instruments' Formal UWB Proposal. In addition, we would like to thank the designers involved in TI's UWB RFIC Program.

- Jaiganesh Balakrishnan
- Anuj Batra
- Anand Dabak
- Ranjit Gharpurey
- Paul Fontaine
- Jerry Lin
- Simon Lee
- Danielle Griffith
- Joel Garza


2

## Scope of Presentation

- A Brief Overview of UWB
- Multi-band OFDM System Characteristics
  - Non-Linearity
  - Band Width
  - Noise
- Architectures for VCO, Synthesizer, RX & TX
  - Frequency Generation Solutions, VCO & PLL
    - Spurs & Multi Pico Nets
  - Base Band Filters
  - Receive RF, Analog & ADC
  - Transmit RF, Analog & DAC
- RF Digital Isolation for SOC Implementation
  - Cross Talk

3

## MBOA UWB Band Plan

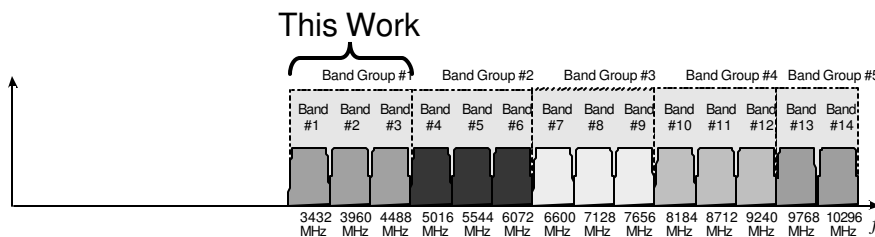


### “Lowest 3 Band” Solutions

- Best Channel Characteristics
- Simplest Off-Chip Filtering Requirements
- ➔ Earliest Introduction to Market

4
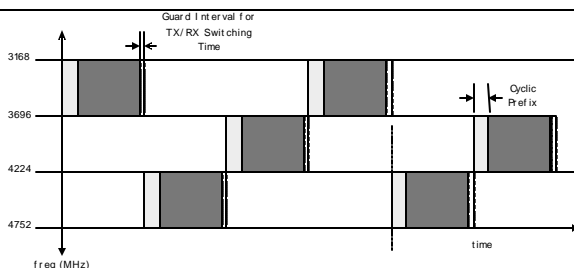
## Overview of Multi-band OFDM


- Basic idea: divide the spectrum into channels that are 528 MHz wide.
- Transmitter and Receiver Process Smaller Bandwidth Signals (528 MHz).
- Insert a 2nS Guard Interval Between OFDM Symbols to Allow Sufficient Time to Switch RFIC Between Channels.
- Each Channel has 128 Sub Carriers 4.25MHz Apart
- 3X Power 1/3 of the Time



5
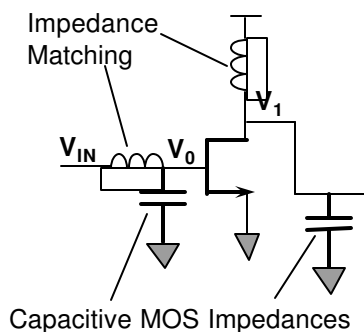
## Low Power & Low Noise RF CMOS

4GHz:  $NF_{min} < 1\text{dB}$  @ 16dB Gain



**RF CMOS Higher Reactive Impedances**  
**→ Narrower Band Widths Improve RF**

- $V_0 \sim V_{IN} X Q_{IN}$
- $V_1 \sim I_{SIG} X Q_L$
- Input S/N  $\sim V_0 \sim Q$
- Gain  $\sim V_1 \sim Q$
- $I_{Bias} \sim 1/Q$

**→ Inductors (Q = 2) Can Improve Noise and Lower Power**

**Inductively Biased Nodes Allow Voltage Swings Outside the Supply Rails**

**→ Higher Dynamic Range**

**Base Band Op Amps Use Feed Back To Improve Performance**


**→ Narrower Band Widths**

**Easy Migration to System on a Chip**

6
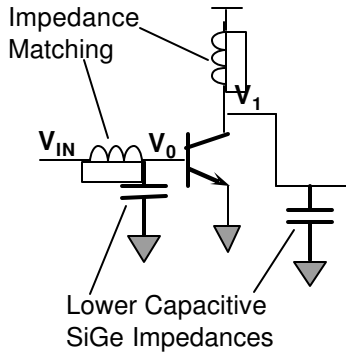
## Low Power & Low Noise RF SiGe

4GHz:  $NF_{min} < 1\text{dB}$  @  $>16\text{dB}$  Gain



**RF SiGe: Lower-Q, Smaller RF Impedances → High Performance RF Well Suited for Broad Band**

- $V_0 \sim V_{IN} X Q_{IN}$
- $V_1 \sim I_{SIG} X Q_L$
- Input S/N  $\sim V_0 \sim Q$
- Gain  $\sim V_1 \sim Q$
- $I_{Bias} \sim 1/Q$

→ Inductors ( $Q = 2$ ) Can Still Improve Noise and Lower Power  
**Inductively Biased Nodes Support Voltage Swings Outside the Supply Rails**


→ Higher Dynamic Range

**Very Good Base Band Amps with Low Gains & Broad Band Widths**


→ Lower Amounts of Feed Back

7

## UWB Solutions: 3168MHz to 4752GHz

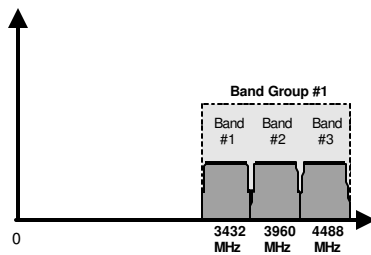

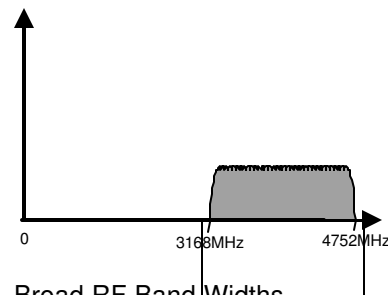- Narrow Instantaneous RF Band Widths
- Lower Converter Sampling Rates
- Base Band Filters/VGA's
  - Lower-Q
  - Smaller Band Width
- 4.25 MHz Carrier Spacing/No Zero Tone
  - No  $1/f$  Noise
- CMOS Friendly System Requirements



- Broad RF Band Widths
- Broad Base-Band Band-Widths
- Higher-Q Base-Band Filters
- High Converter Sampling Rates
- SiGe Friendly System Requirements


8

## MBOA UWB: Distortion Floor for TX/RX

2<sup>nd</sup> and 3<sup>rd</sup> Order “Beats” Set Inter-Modulation Distortion Floor in MBOA UWB

$$V_{in} = V_A \cos(a) + V_B \cos(b) + V_C \cos(c)$$
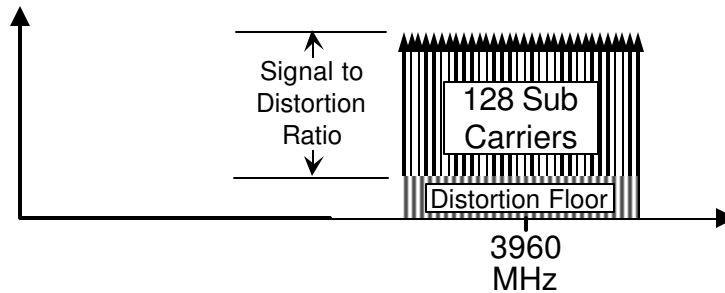
$$V_{out} = \underbrace{k_1 V_{in}}_{\text{Signal}} + \underbrace{k_2 V_{in}^2 + k_3 V_{in}^3}_{\text{Distortion}}$$




9

## 3<sup>rd</sup> Order Inter Modulation Floor: 128 Sub Carriers

$$V_{IN} = A \cos(a) + B \cos(b) + C \cos(c)$$

$$V_{OUT} = k_1 V_{IN} + k_2 V_{IN}^2 + k_3 V_{IN}^3$$
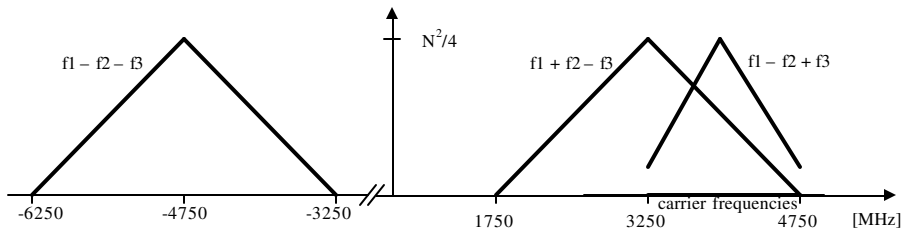
$$k_3 V_{IN}^3 = k_3 \left[ \frac{1}{4} A^3 \cos(3a) + \frac{1}{4} B^3 \cos(3b) + \frac{1}{4} C^3 \cos(3c) + \frac{3}{4} A^2 B \cos(2a \pm b) + \frac{3}{4} A^2 C \cos(2a \pm c) + \frac{3}{4} B^2 A \cos(2b \pm a) + \frac{3}{4} B^2 C \cos(2b \pm c) + \frac{3}{4} C^2 A \cos(2c \pm a) + \frac{3}{4} C^2 B \cos(2c \pm b) + \frac{3}{2} ABC \cos(a \pm b \pm c) \right]$$



- Triple beats are 6dB higher than two-tone IM3 products
- Many more triple beats than IM3 products
- ~  $3N^2/8$  beats near middle of band
- ~  $N^2/4$  product terms near edge of band
- $CTB(dBc) = IM3(dBc) + 6 + 10 \log(3N^2/8)$


10

## UWB Second Order Inter Modulation Floor

$$V_{IN} = A \cos(a) + B \cos(b) + C \cos(c)$$

$$V_{OUT} = k_1 V_{IN} + k_2 V_{IN}^2 + k_3 V_{IN}^3$$
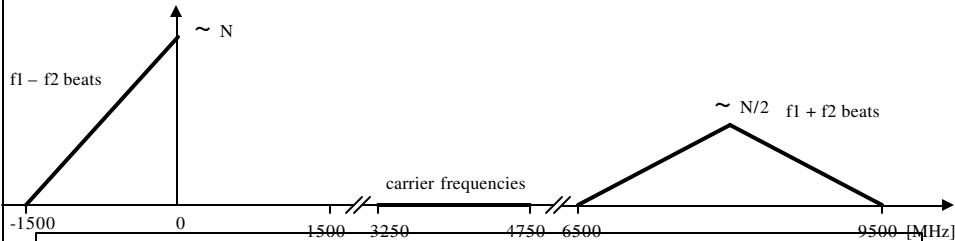
$$k_2 V_{IN}^2 = \frac{1}{2} k_2 A^2 + \frac{1}{2} k_2 B^2 + \frac{1}{2} k_2 C^2 + k_2 AB \cos(a \pm b) + k_2 AC \cos(a \pm c) + k_2 BC \cos(b \pm c) + \frac{1}{2} k_2 A^2 \cos(2a) + \frac{1}{2} k_2 B^2 \cos(2b) + \frac{1}{2} k_2 C^2 \cos(2c)$$



- CSO products are out of band in RF path
- Generate Signal dependent DC offsets at LNA output
- Reduced By Low-Q L-C Filtering Before Down Conversion

11

## Multi-Band OFDM System Parameters

Info. Data Rate	110 Mbps	200 Mbps	480 Mbps
Modulation/Constellation	OFDM/QPSK	OFDM/QPSK	OFDM/QPSK
FFT Size	128	128	128
Coding Rate (K=7)	R = 11/32	R = 5/8	R = 3/4
Spreading Rate	2	2	1
Information Tones	50	50	100
Data Tones	100	100	100
Info. Length	242.4 ns	242.4 ns	242.4 ns
Cyclic Prefix	60.6 ns	60.6 ns	60.6 ns
Guard Interval	9.5 ns	9.5 ns	9.5 ns
Symbol Length	312.5 ns	312.5 ns	312.5 ns
Channel Bit Rate	640 Mbps	640 Mbps	640 Mbps
Frequency Band	3168 – 4752 MHz	3168 – 4752 MHz	3168 – 4752 MHz
Multi-path Tolerance	60.6 ns	60.6 ns	60.6 ns

- 1) Tolerant of Inter-Mods, Image, and Synthesizer Noise
- 2) Fast Synthesizer 9.5nS for System → ~ 2nS for RFIC
- 3) Short “In-Channel” Settling Times for RFIC
- 4) Frequencies Readily Obtained on CMOS RFIC

12

# Link Budget and Receiver Sensitivity

Assumption: AWGN and 0 dBi gain at TX/RX antenna


Parameter	Value	Value	Value
Information Data Rate	110 Mb/s	200 Mb/s	480 Mb/s
Average TX Power	-10.3 dBm	-10.3 dBm	-10.3 dBm
Total Path Loss	64.2 dB (@ 10 meters)	56.2 dB (@ 4 meters)	50.2 dB (@ 2 meters)
Average RX Power	-74.5 dBm	-66.5 dBm	-60.5 dBm
Noise Power Per Bit	-93.6 dBm	-91.0 dBm	-87.2 dBm
RX Noise Figure	6.6 dB	6.6 dB	6.6 dB
Total Noise Power	-87.0 dBm	-84.4 dBm	-80.6 dBm
Required Eb/N0	4.0 dB	4.7 dB	4.9 dB
Implementation Loss	3.0 dB	3.0 dB	3.0 dB
Link Margin	5.5 dB	10.2 dB	12.2 dB
RX Sensitivity Level	-80.0 dBm	-76.7 dBm	-72.7 dBm

- 1) Very Low TX Power → Fully Integrated PA
- 2) 6.5dB for switch + filter + receiver → ~ 4.5dB for RFIC
- 3) Tolerant of Inter-Mods, Image, and Synthesizer Noise

13
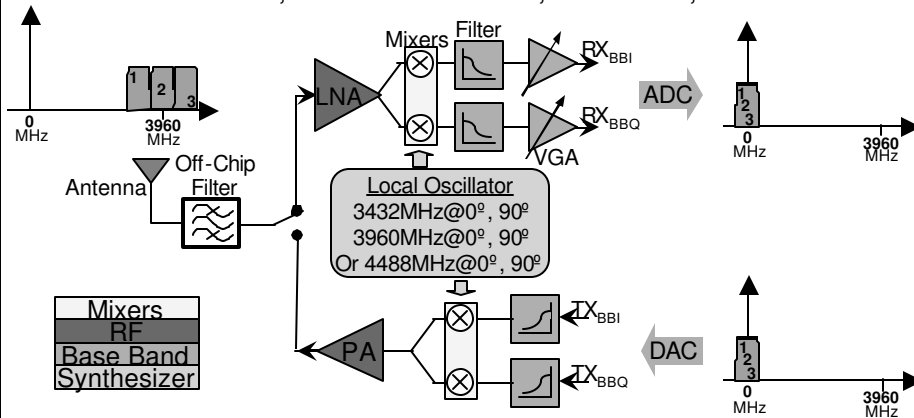
# Direct Conversion UWB Transceiver

Low Power, Low Noise ~ 4dB, Low Cost, 480MBPS



**Channel Switching Time ~ 2nS (~10,000 Times Faster Than 802.11)**

→ Complex Frequency Synthesis & Frequency Conversion

**Low TX Power ~ -10dBm RMS**


→ Fully Integrated PA

→ Very Low Noise RFIC Required NF ~ 4dB

14
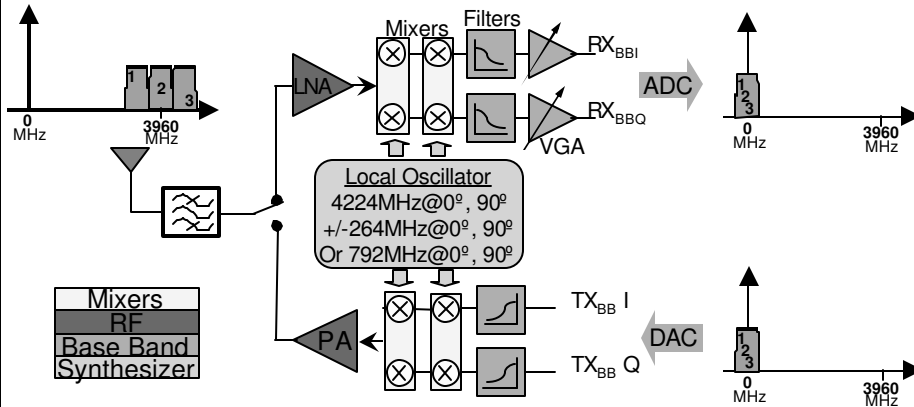
# Direct Conversion UWB Transceiver

Low Power, Low Noise ~ 4dB, Low Cost, 480MBPS



**Channel Switching Time ~ 2ns, Two RF LO Frequencies Needed**

→ Unique Frequency Synthesis & Frequency Conversion

**Low TX Power ~ -10dBm RMS**

→ Fully Integrated PA

**More Complex Dual Stage RX/TX → Simpler Frequency Synthesis**

15

# MBOA UWB: Frequency Synthesis

- Fast Frequency Hopping
  - Necessary condition for multi-band proposals
  - Frequency switching time < 2ns
- Standard Closed Loop PLL Design is Far Too Slow
- Frequency Synthesis Using Single-Sideband Generation
- All Frequencies Derived From Multiples of 16MHz
  - All IC cells fully synchronous
    - ADC outputs, mixer LOs, RX & TX digital base band, ...

16




# Frequency Synthesis

(Generating 3 Frequencies from 1)

- VCO center frequency = 4224MHz = 264 x 16MHz
  - 4224 MHz ÷ 4 output = 1056MHz, ÷ 16 output = 264MHz
- Single sideband generation principle: 2 = Sine Wave
  - $\cos(\omega_1 t) \times \cos(\omega_2 t) - \sin(\omega_1 t) \times \sin(\omega_2 t) = \cos[(\omega_1 + \omega_2)t]$
  - $\cos(\omega_1 t) \times \sin(\omega_2 t) + \sin(\omega_1 t) \times \cos(\omega_2 t) = \sin[(\omega_1 + \omega_2)t]$
  - $\cos(\omega_1 t) \times \cos(\omega_2 t) + \sin(\omega_1 t) \times \sin(\omega_2 t) = \cos[(\omega_1 - \omega_2)t]$
  - $\cos(\omega_1 t) \times \sin(\omega_2 t) - \sin(\omega_1 t) \times \cos(\omega_2 t) = \sin[(\omega_1 - \omega_2)t]$
  - Unwanted Frequency Rejected ~ 30dB
- All three frequencies can be generated rapidly
  - 792MHz = 1056MHz – 264MHz
  - Channel 1: 4224 - 792 = 3432MHz
  - Channel 2: 4224 - 264 = 3960MHz
  - Channel 3: 4224 + 264 = 4488MHz


17
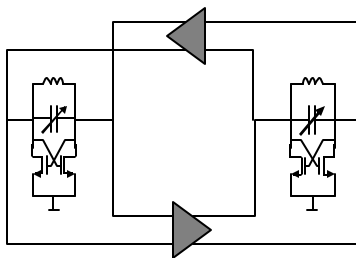
## Quadrature Voltage Controlled Oscillators



Ring Oscillator

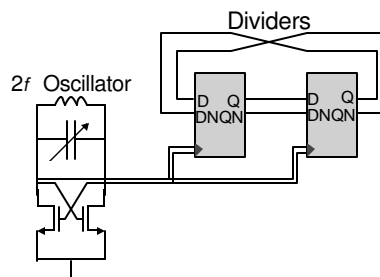- Quadrature Output VCO
  - No Separate Phase Splitter
- Lower Operating Frequency
  - Better Yield?
- Variable MOS capacitors set frequency to 4224MHz



2f Oscillator (8448MHz)

- Reduced 1f Radiation
- Reduced VCO Pulling
- Smaller Implementation
- Higher Inductor Q's


Two-Stage D<sub>Flip-Flop</sub> Dividers

- Divided Clocks in Quadrature

18
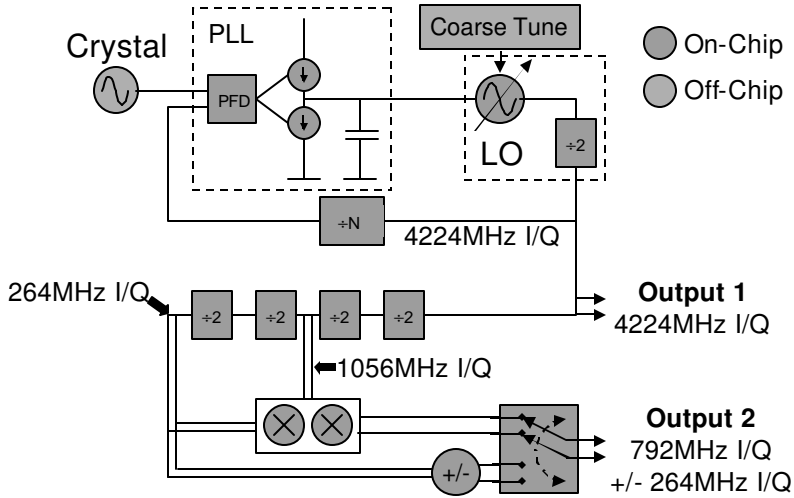
## UWB Synthesizer Dual Output Frequency


Channel Select  $\sim 2\text{nS}$ ; Outputs:  $f_1=4224\text{MHz}$ ,  $f_2 = +/-264$  Or  $792\text{MHz}$



19

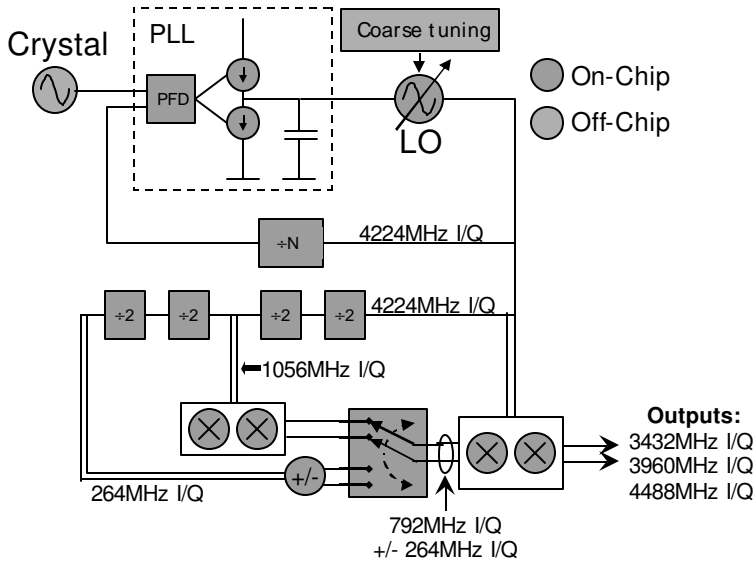
## UWB Synthesizer: Single Output Frequency

Channel Select  $\sim 2\text{nS}$ ; Outputs: 3432, 3960 Or 4488MHz



20
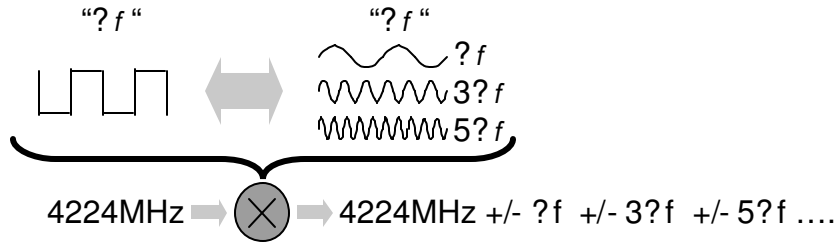
## “Non-Linear” Frequency Conversion: Spurs!



Single sideband generation principle:  $? f = \frac{?}{2\pi} = \text{Square wave}$

$$\{\cos(\omega_1 t) \times \cos(\omega_2 t) - \sin(\omega_1 t) \times \sin(\omega_2 t)\} = \cos[(\omega_1 + \omega_2)t]$$

$$+ \{\cos(\omega_1 t) \times \cos(3\omega_2 t) + \sin(\omega_1 t) \times \sin(3\omega_2 t)\} = \frac{\cos[(\omega_1 - 3\omega_2)t]}{3}$$

$$+ \{\cos(\omega_1 t) \times \cos(5\omega_2 t) + \sin(\omega_1 t) \times \sin(5\omega_2 t)\} = \frac{\cos[(\omega_1 + 5\omega_2)t]}{5} + \dots$$


$$\rightarrow ?f_{264} = 264\text{MHz} \ \& \ -792\text{MHz} \ \& \ 1320\text{MHz} \ \& \ \dots$$

$$\rightarrow ?f_{792} = 792\text{MHz} \ \& \ -2376\text{MHz} \ \& \ \dots$$

- Channel 1 Output = 3432MHz, 6600MHz, 264MHz, ...
- Channel 2 Output = 3960MHz, 5016MHz, 2904MHz, ...
- Channel 3 Output = 2376MHz, 3432MHz, 4488MHz, ...

21

## LO Spurious & Multiple Pico Nets

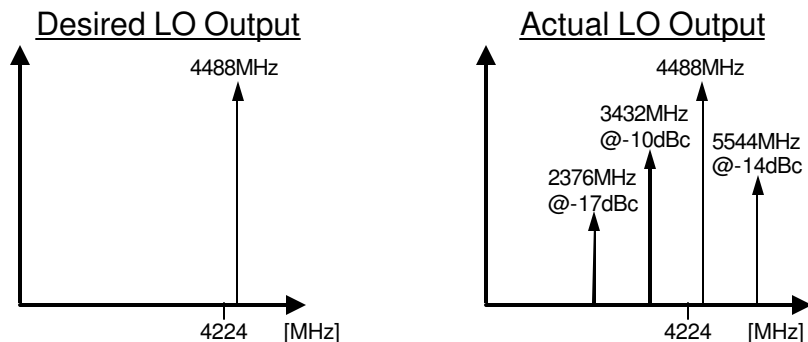

### LO Spurious

- Mix Channel 1 on Top of Channel 3
- Transmit on Channel 1 When Channel 3 is Selected
- ➔ Prevent Coexistence of Multiple Pico-Nets
- Mix Undesired Wireless Standards Into UWB Receive Bands
- Transmits UWB Data Into Spectrum Allocated to Other Standards
- ➔ Hampers Coexistence with Other Wireless Standards

22

## Base Band Filters

### RX Channel Select Filter (528MSPS ADC)

- 3<sup>rd</sup> Order All Pole Response
- $F_c \sim 250\text{MHz}$
- On-Chip Auto Tuning of Filter Corner
- Filter can be integrated into the VGA
  - Real pole at Output of Mixer
  - Complex pole can be combined with VGA Op-Amp


### TX Image Reject Filter (1056MSPS DAC)

- Second Order Response
- +0 to +1dB @ 250MHz
- Auto Tuning of Filter Corner

23

## MBOA UWB Base Band Filters

(One-Half of Differential Section Shown)

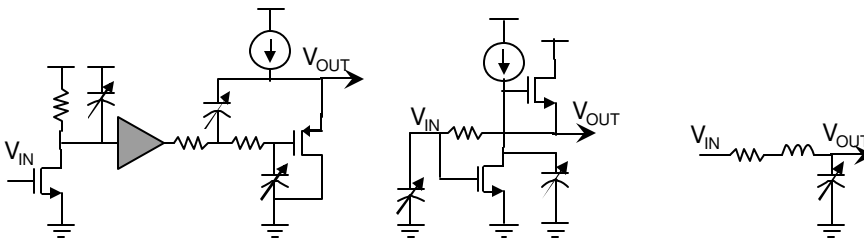

### Sallen & Key

Low-Q  
Stable  
Moderate power  
Requires Buffer  
No Voltage Gain

### Op-Amp Based


Higher-Q  
Stability Issues  
Moderate Power  
Low-Z Drive  
Has Gain

### L-C

Moderate-Q  
Most Stable  
Zero power  
Requires Buffer  
No Gain

24

## Base Band Self-Calibration: Example

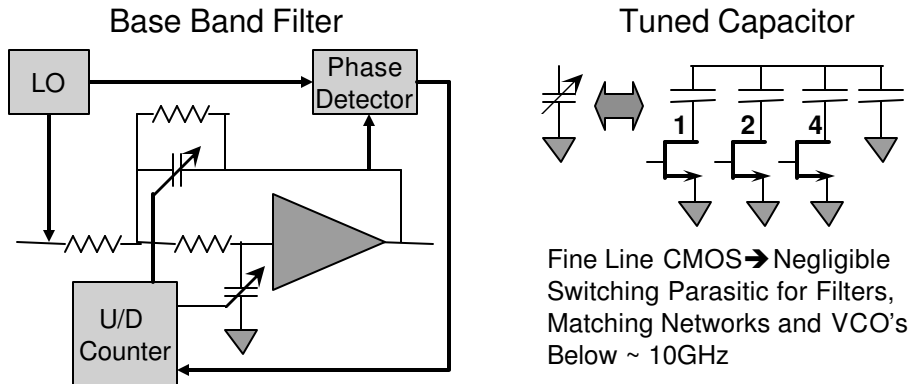


### Filter Self-Calibration

- Higher Yield & Lower Costs
- Higher Realized Performance
- RF/Analog Self Testing at DC Probe

25


## ADC Spec/Issues for UWB Receiver

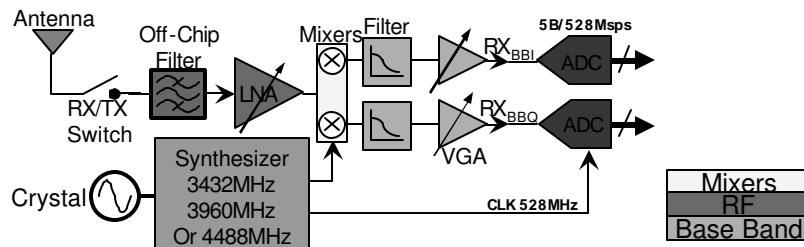

- ADC:
  - **5bits/528MHz**
  - Power Hungry Component in UWB
- VGA & Base Band Filters
  - Large Gain Range
  - Flat Response to ~ 240MHz
  - Can Combine Base Band Filters With Gain Blocks
  - May Need 50 Ohm Drive
- More Complex Synthesizer → LO Spurs
- Standard Receive Mixers
- Gain Step in LNA

26

## ADC Spec/Issues for UWB Receiver

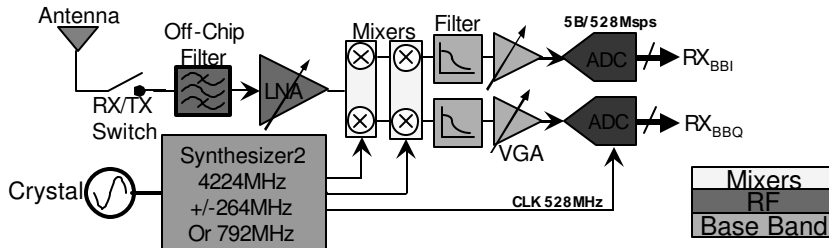


- ADC:
  - 5bits/528MHz
  - Power Hungry Component in UWB
- VGA & Base Band Filters
  - Large Gain Range
  - Flat Response to ~ 240MHz
  - Can Combine Base Band Filters With Gain Blocks
  - May Need 50Ω Drive
- Less Complex Synthesizer
- Dual Stage Receive Mixers → LO Spurs
- Gain Step in LNA


27
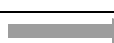
## Basic Flash ADC

Continuous time signal  
with infinite resolution



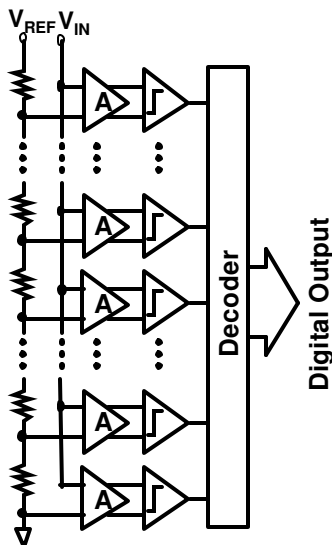Discrete time signal with  
finite resolution



### Structure


- Input Capacitance ~  $2^{\#}$  of Bits
- Pre-Amps & Comparators ~  $2^{\#}$  of Bits
  - Area & Power ~  $2^{\#}$  of Bits
- Sample & Hold Not Required

### Performance Issues

- Input Feed-Through to Reference
- Comparator Kickback
- Clock Jitter

28

## Transmitter 1 for MBOA UWB

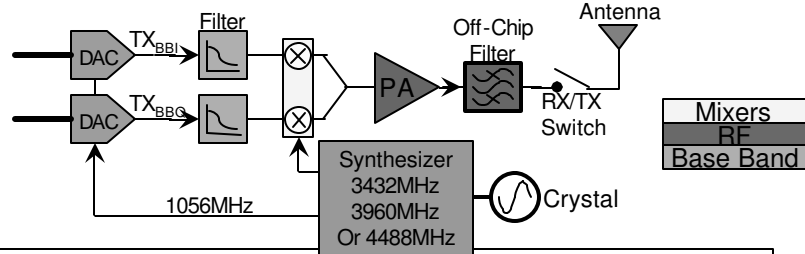


### Requirements

- DAC: 5bits @ 1.056GHz Sampling Rate
- Low pass Filter
  - Flat To ~ 240MHz
  - Suppresses (1056 – 264)MHz and Beyond
- Simple Up-Conversion Mixers
- A Single RF Output Synthesizer
  - Shared with DAC & Receiver
  - Higher Complexity LO Generation → LO Spurs

29

## Transmitter 2 for MBOA UWB

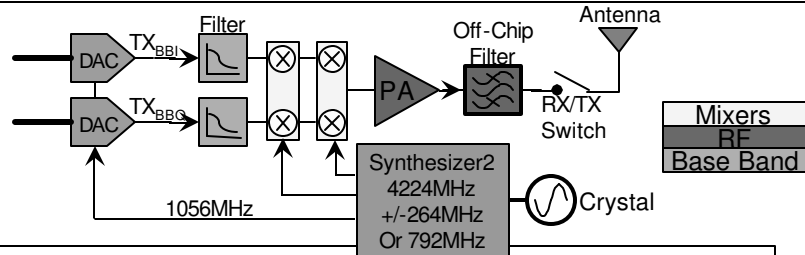


### Requirements

- DAC: 5bits @ 1.056GHz Sampling Rate
- Low pass Filter
  - Flat To ~ 240MHz
  - Suppresses (1056 – 264)MHz and Beyond
- Two Stage Up-Conversion Mixers
  - Spurious Issues
- Simpler Dual RF Output Synthesizer
  - Shared with DAC & Receiver
  - Switching Time < 2ns

30


# Band Set #1 Emission Mask Proposal

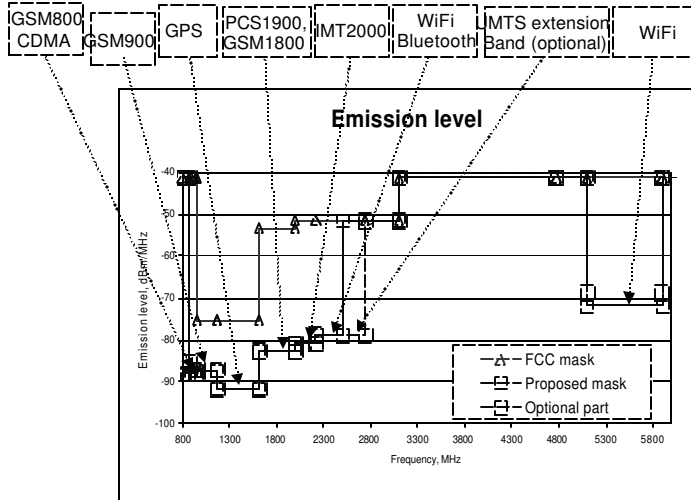

31
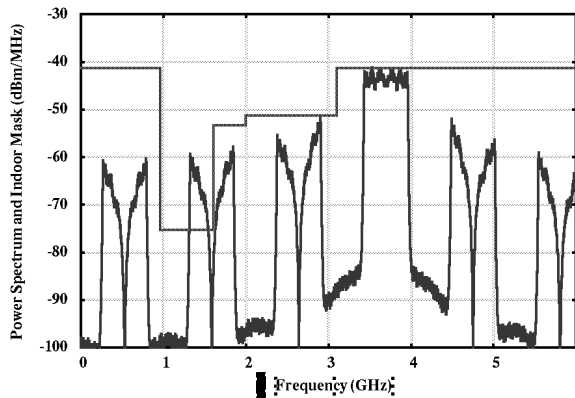
# TX Base Band Output Spectrum: No Filter

- High level simulation (DAC and mixer)
- 2<sup>nd</sup> left sided image in GPS band Violates TX Mask




32



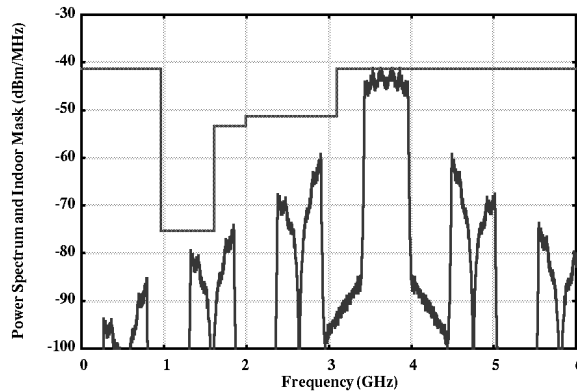
## Base Band Output Spectrum with Filtering

- Simple Low-pass filter → 5dB Margin
- Additional RF Filtering Improves Margin




33

## UWB Transceiver Design Approach

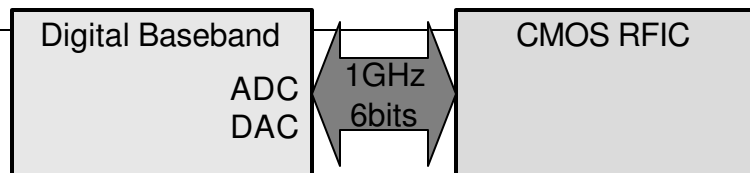

Next Generation (SoC)

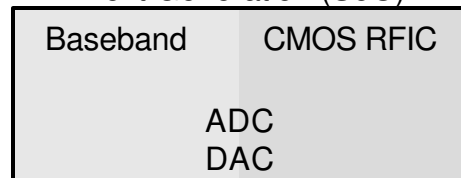

Multi-Chip to Full System on a Chip

- Self Calibration: RF/VCO/Analog Base Band
- Cross Talk Suppression: System & Design Level

34

# System on a Chip

## Advantages


- Reduced Implementation Cost
- Improved Vendor Acceptance

## Challenges

- Cost of Lower Yield
- Device Modeling
- Cross Talk

35

## Cross Talk

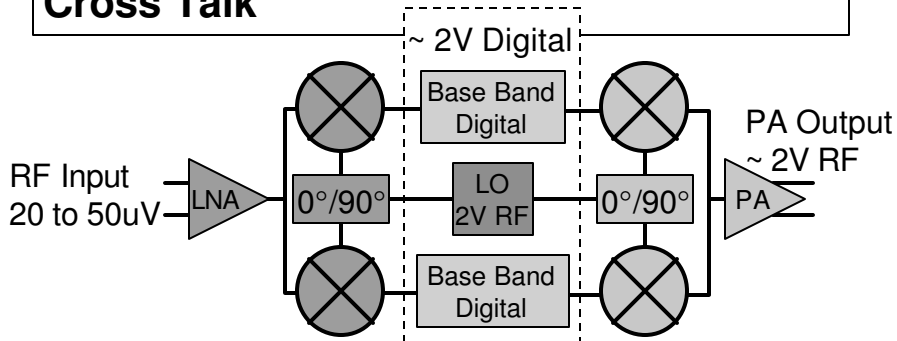


## On-Chip Coupling

- TX Output/Harmonics Pull VCO
- Strong RF Input/Harmonics Pull VCO
- Digital Contaminates Base Band or RF
- Digital Over-Drives RF or Base Band Input
- TX Output Over-Drives RX Input (UMTS)
- TX/RX Mode Changes "Kick" VCO
- VCO Feed Through Violates FCC Max Power

36

# Inductive Cross Talk

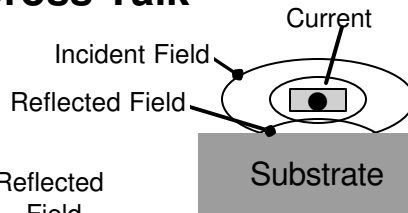

## Inductive Vector Potential:

$$E(f, \rho, z) \propto I \int_0^\infty \frac{dk_\rho k_\rho}{k_z} J_0(k_\rho \rho) \left[ e^{ik|z-z'|} + Ae^{-ik_z z} \right], \quad f = \frac{c}{2\pi} \sqrt{k_\rho^2 + k_z^2}$$

Incident Field  
Reflected Field

$$E(2GHz, \rho, z) \Rightarrow \frac{6 \cdot 10^3 V}{\rho(\mu m)} + \left[ \begin{array}{c} 40 \\ 20 \\ 0 \\ -20 \\ -40 \end{array} \right] \left[ \begin{array}{c} \text{Im}|E| \\ \text{Re}|E| \end{array} \right] \rho(\mu m)$$

The graph shows the imaginary part of the electric field (Im|E|) and the real part (Re|E|) as a function of distance rho in micrometers. The y-axis ranges from -40 to 40 V/m, and the x-axis ranges from 0 to 400 micrometers. Im|E| starts at approximately 30 V/m at rho=0 and decays towards 0. Re|E| starts at 0 at rho=0 and increases linearly to approximately -30 V/m at rho=400 micrometers.


Static Component

Dynamic Component:  
Weakly Spatially Dependent

37

# Magneto Static Cross Talk

(No Simple Board Level Solution)

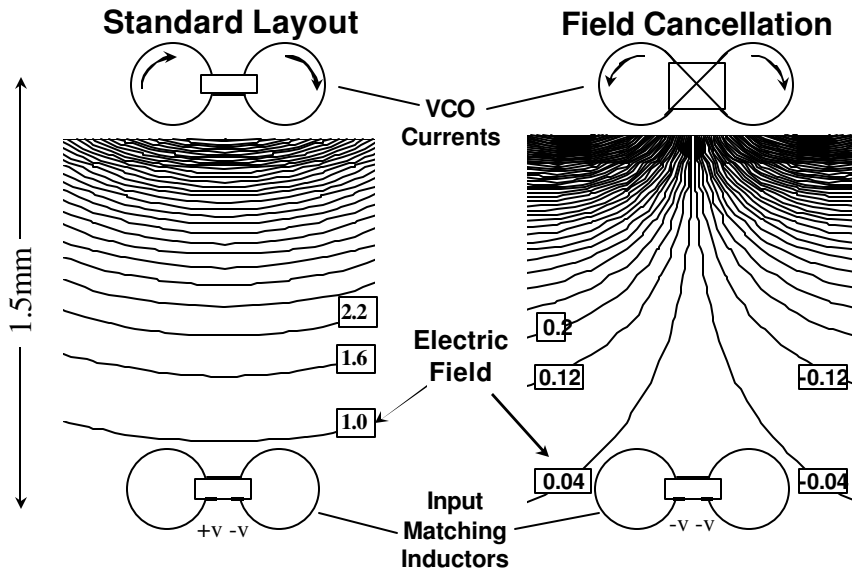


38


# Cross Talk Suppression

## Electro Magnetic Isolation

Standard Layout

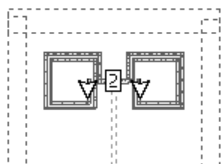

Anti-Symmetric Layout

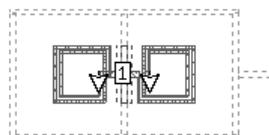

Anti-Symmetric Layout: ~ 20dB More Isolation

## System Level & On-Chip Cross Talk Suppression

- Digital Spectral Content Far From RF
- VCO Electromagnetically Isolated and Resistant to LF Pulling
- LNA Input Narrow Band and Electromagnetically Isolated
- Layout/Floor Plan Optimized with Electromagnetic Solver

39

# Electrostatic Cross Talk

## Shielded Scalar Potential:


$$\phi_i \sim q \int \frac{1}{|\vec{r}_i - \vec{r}_j|} - \frac{1}{|\vec{r}_i - \vec{r}_j - 2z\hat{z}|} dl_j$$

- Frequency Independent
- Decreases Rapidly for  $|\vec{r}_i - \vec{r}_j| > 2z \sim 10\mu m$

## Shielding Requirements:

$$R_{\text{Shield}} \ll R_{\text{Substrate}} \text{ with } C_{\text{parasitic}} \times [R_{\text{Shield}} || R_{\text{Substrate}}] \ll (2\pi f)^{-1}$$
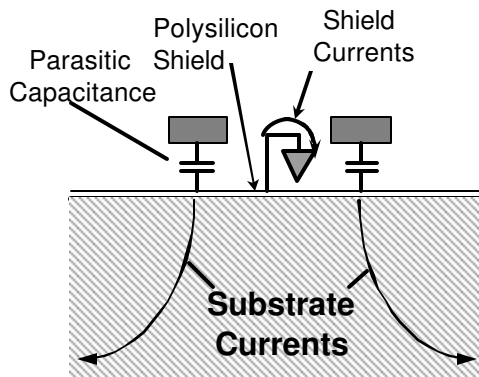
$$R_{\text{Substrate}} \sim \frac{\rho_{\text{Substrate}}}{4\pi} \int_{\sqrt{A/4\pi}}^{\infty} \frac{1}{r^2} dr$$



Parasitic Currents are Shunted to Ground Through Low Loss Substrate Shielding  
 ➤ Improves Q  
 ➤ Greatly Reduces Cross Talk

40

## Conclusion

- MBOA UWB Was Developed for a High Performance CMOS Implementation.
- VCO Core Requirements & Many RX/TX Requirements are More Relaxed Than Other Wireless Standards.
- LO Spurious Requirements for MBOA UWB and Base Band Bandwidth are the Primary Design Challenges
- MBOA UWB Was Developed for a Direct Migration to Full, Low-Cost System on a Chip

41