

Fully Integrated Switched-Capacitor DC-DC Conversion


Elad Alon

In collaboration with Hanh-Phuc Le, Seth Sanders




**Berkeley Wireless Research Center
University of California, Berkeley**


Multi-Core Chips Are Here

 

Intel Westmere

 

AMD Phenom

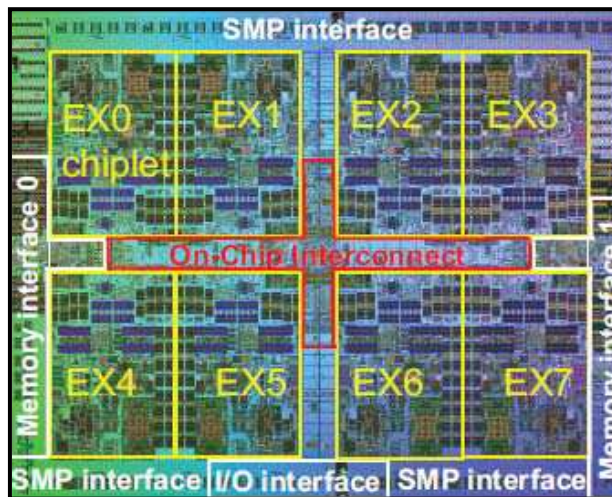

IBM POWER7



Sun Rainbow Falls



Multi-Supply Chips?

- **Separate supply voltages clearly desirable**
 - Power management, compensate variability, etc.
- **But, true multi-supply adoption slow**
 - Except for power gating
- **Why not use multiple external converters?**




Shin, ISSCC 2010

Supply Impedance and Split Planes

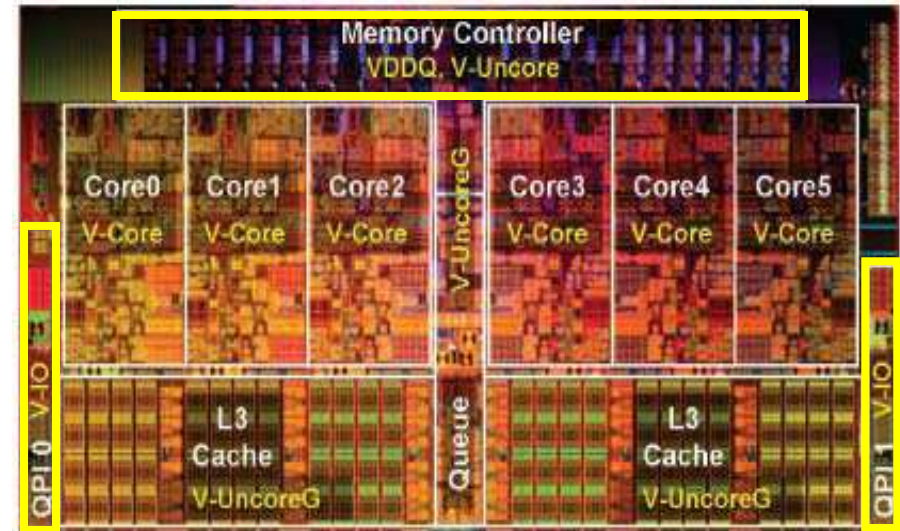 

- **Supply impedance requirement extremely low**
 - 1V, 100A part \rightarrow 1m Ω
- **Split power planes bad for impedance**
 - Load and decap isolation
 - Reason I/O's often placed on edges even with flip-chip



On-Die Voltage Conversion

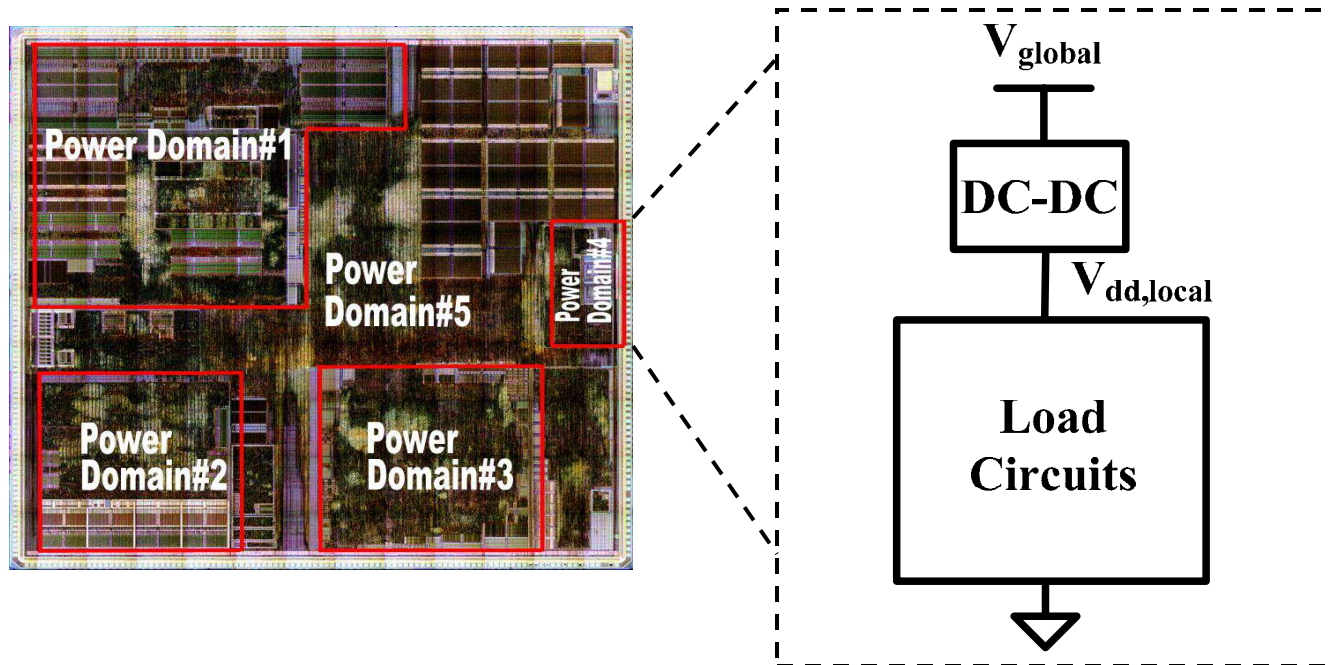

- **Enables single, low-impedance global input voltage**
- **Key challenge: fully integrated DC-DC**
 - Energy storage must be integrated on-die too



Switching Converter Options

Inductor:

  

- Conversion ratio set by duty cycle
- Very popular for off-chip converters


Capacitor:

  

- Conversion ratio set by topology
- Many perceived disadvantages



So Why Switched-Capacitor (SC)?

 - **Key motivation:**
integration with low cost
 - Dense, high-quality capacitance widely available
 - (Development of on-die magnetics can be leveraged for SC converters too)




- **Integrated SC design can mitigate perceived downsides**
 - Component count no longer critical
- **What is achievable efficiency, power density?**

Selected Previous Designs


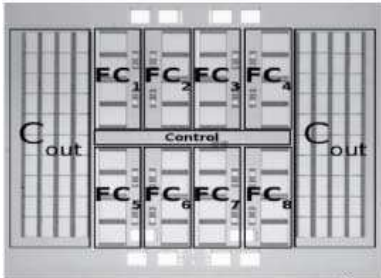
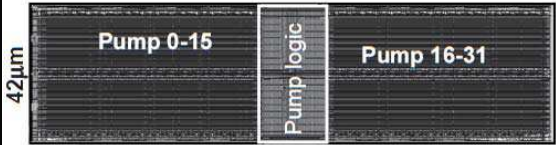
Work	Breussegem, VLSI 09	Somasekhar, VLSI 09
Technology	130nm Bulk	32nm Bulk
Topology	2/1 step-up	2/1 step-up
Interleaved Phases	16	32
Converter Area (mm ²)	2.25	6.678x10 ⁻³
Power density @ η_{\max}	0.002 W/mm ²	1.123 W/mm ²
Efficiency (η_{\max})	82%	60%
		

Review: SC Basics

Phase 1:

 


Phase 2:

   


Switched Capacitor (SC) Basics

Phase 1:

 


Phase 2:

 

- Conversion ratio set by topology
- Works in other direction too
 - Step-up: reverse V_i , V_o

SC Converter Loss Mechanisms

 

- **Intrinsic loss**
 - Fundamental to converter operation
- **Switch/parasitic loss**
 - Non-idealities of the capacitor(s) and switches


SC Converter Loss with Digital Loads

- Gate delay depends on V_{dd} :
 - Performance set by V_{min}

- SC converter effective output resistance (for V_{min}):

$$R_{eff,Csw} = \frac{1}{M_{conv,cap} C_{conv} f_{sw}}$$

$$V_{min} = \frac{V_i - \Delta V}{2}$$

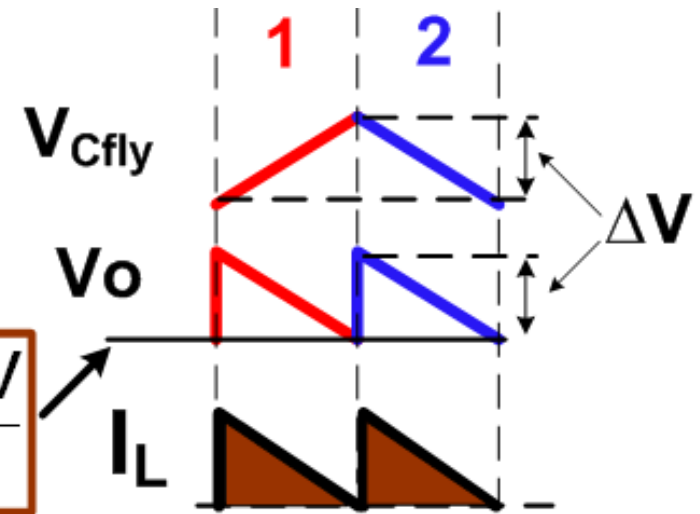

- But, load also draws “extra” current when $V_{dd} > V_{min}$
 - This power is wasted since it doesn’t improve performance

- Ripple leads to extra loss: $P_{Reff} = \frac{2 I_{load}^2}{M_{conv,cap} C_{conv} f_{sw}}$

Interleaving


- **Good news: interleaving reduces ripple**

- But leaves V_{\min} unchanged


- **With N_{int} interleaved converters:**

$$P_{\text{Reff}} = \left(1 + \frac{1}{N_{\text{int}}}\right) \frac{I_{\text{load}}^2}{M_{\text{conv,cap}} C_{\text{conv}} f_{\text{sw}}}$$

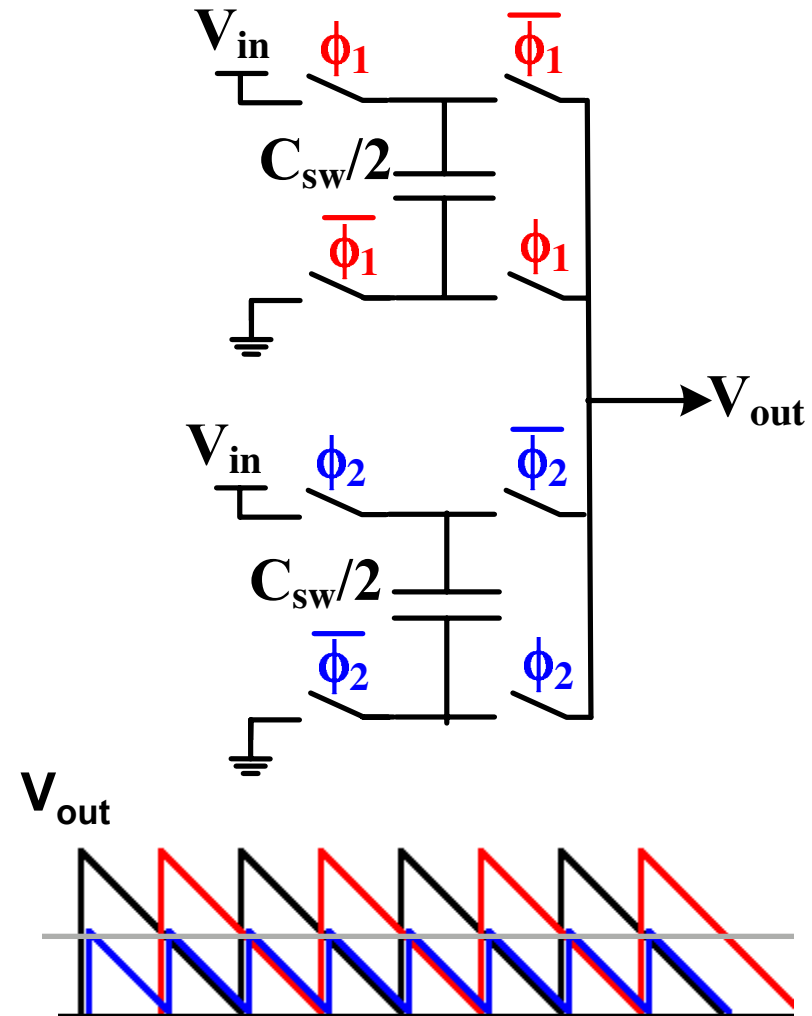- **Ripple minor for ~16+ way interleaving**





Efficiency Optimization

 

- **Intrinsic loss**
 - Reduced by \uparrow C density
 - Reduced by $\uparrow f_{sw}$
- **Switch/parasitic loss**
 - Reduced by \uparrow switch f_T
 - Increased by $\uparrow f_{sw}$
- **Efficiency optimization: choose f_{sw} and W_{sw} to balance loss terms**

Loss Terms Detail

  

Sw.-cap R:

$$P_{Reff} \approx \frac{I_{load}^2}{M_{ccap} C_{conv} f_{sw}}$$

Switch R:

$$P_{Rsw} = \frac{M_{sw} I_{load}^2 R_{on}}{W_{sw}}$$

Bottom plate:

$$P_{Cbot} = M_{bott} C_{bot} V_{out}^2 f_{sw}$$


Gate loss:

$$P_{Csw} = W_{sw} C_{sw} V_{sw}^2 f_{sw}$$

Optimized Efficiency

- Ignoring bottom-plate:

 
$$\frac{P_{loss}}{P_{load}} = 3 \cdot \sqrt[3]{M_{conv,sw} M_{conv,cap} \frac{V_{sw}^2 R_{on} C_{sw}}{V_{out}^2 R_L C_{conv}}}$$




Optimized Efficiency cont'd

- **Efficiency set by *conductance density***
 - I.e., $(I_{load}/V_{out}) / \text{Conv. Area}$
 - (Equivalent to power density for given V_{out})
- **Typical numbers (1V)**
 - Mobile device: $\sim 0.1 \text{ S/mm}^2$
 - Processor: $\sim 1 \text{ S/mm}^2$
- **Efficiency trades off with converter area overhead.**
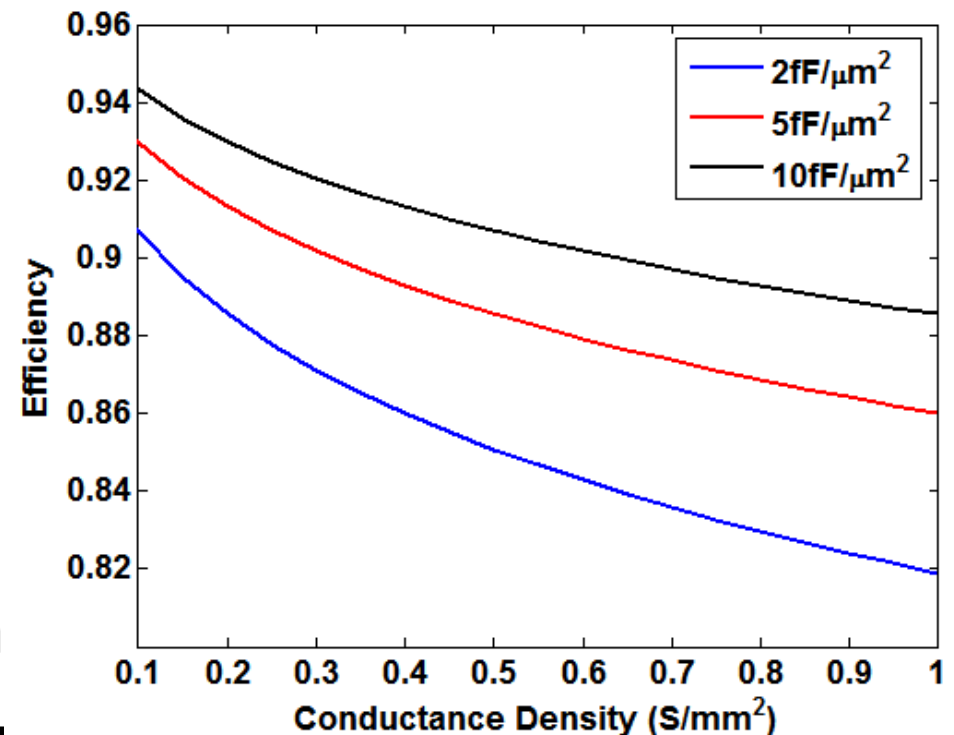
$$\frac{P_{loss}}{P_{load}} = 3 \cdot \sqrt[3]{M_{sw} M_{cap} \frac{V_{sw}^2 R_{on} C_{sw}}{V_{out}^2 R_L C_{conv}}}$$



Side Note

 


- **Explicit decoupling capacitance usually required for supply integrity**
- **Can largely replace decap with converter**
 - In order to fit, converter needs to deliver ~10X higher density than load

Impact of Bottom-Plate

- With $C_{bot} = k_{bot} C_{conv}$:
 
$$\frac{P_{loss}}{P_{load}} = 2\sqrt{M_{cap} M_{bott} k_{bot}} + 2\sqrt{\left(M_{sw} \sqrt{\frac{M_{cap}}{M_{bott} k_{bot}}} \right) \frac{V_{sw}^2 R_{on} C_{sw}}{V_{out}^2 R_L C_{conv}}}$$




Impact of Bottom-Plate cont'd

- Bottom plate sets min. loss:**

- E.g., 2:1 step-down,
1% bottom plate → 10% loss


$$P_{loss} / P_{load} \approx 2\sqrt{M_{cap} M_{bott} k_{bot}}$$

 - **In the limit of low power density:**
- **Converter area does not affect efficiency**
- **Low parasitics more important than cap. density**



Achievable Performance




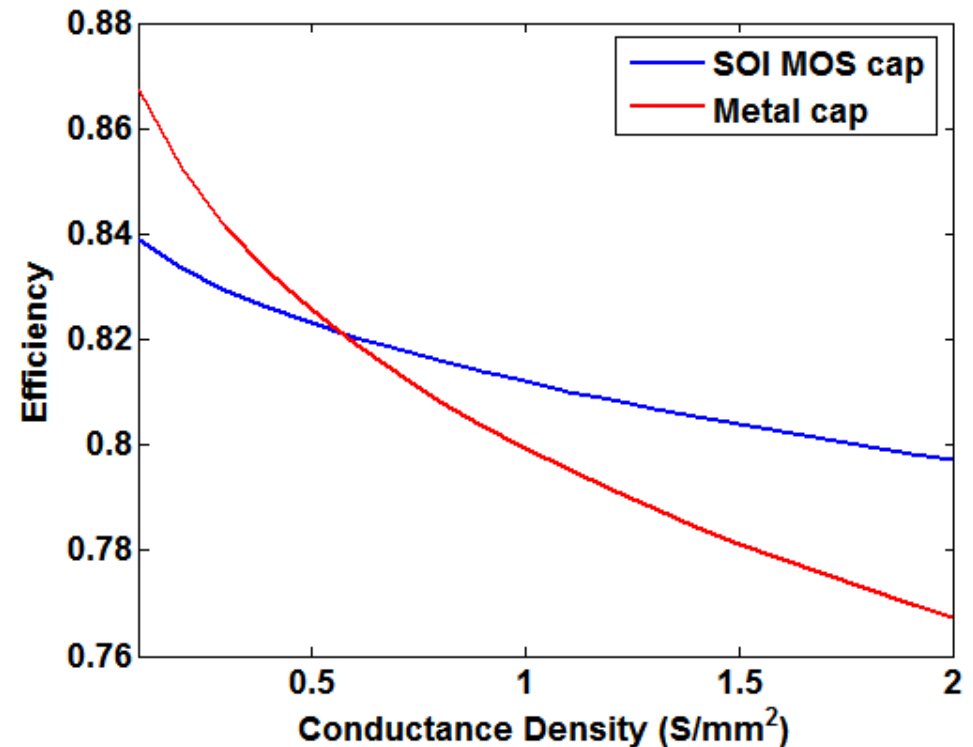
- **45nm, 2:1 converter:**
 - 75% - 80% efficiency at $1\text{W}/\text{mm}^2$
 - Even in standard CMOS
- **Looks promising**
 - Reminder: mobile device $\sim 0.1\text{W}/\text{mm}^2$
 - But, only checked one conversion ratio so far...



- **How to handle variable voltages?**


SC “Standard Cell” Converter

    - Integrated capacitors/switches easily partitioned
- “Standard cell” configuration sets conversion ratio







Efficiency vs. Conversion Ratio

 - **Change topology,**
 W_{sw} , and f_{sw}
 - $R_{out} \sim 1/(Cf_{sw})$
 - Just like linear regulator
- **Probably need only ~4-5 topologies**
 - Clustered around 2:1
 - Watch out for switch drivers





Prototype

   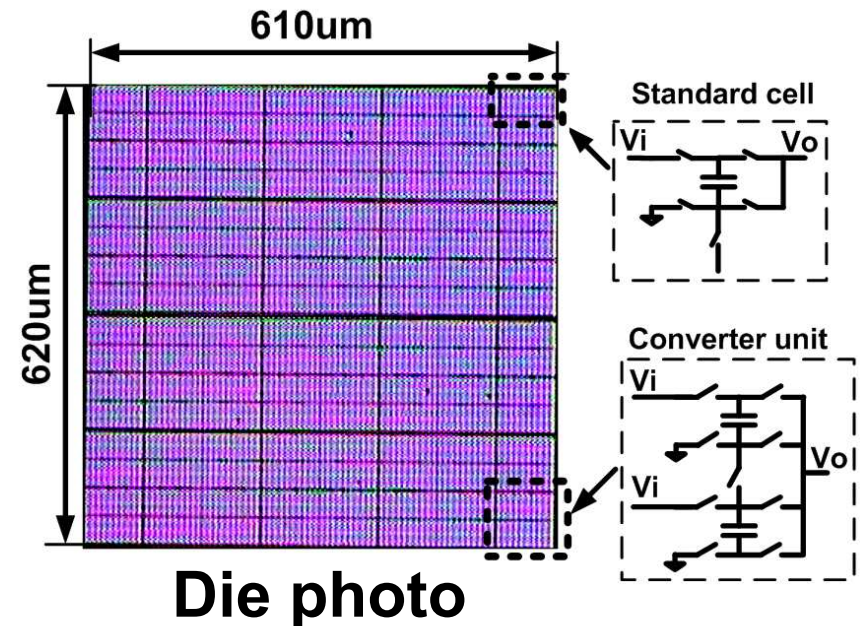- Implemented in 32nm SOI test-chip (w/AMD)
- MOS flying capacitors, 32-way interleaved
- Supports 0.6V ~ 1.2V from 2V input



H.-P. Le, S. Sanders, and E. Alon, "Design Techniques for Fully Integrated Switched-Capacitor DC-DC Converters," *JSSC* Sept 2011.


Measured Efficiency vs. Power Density

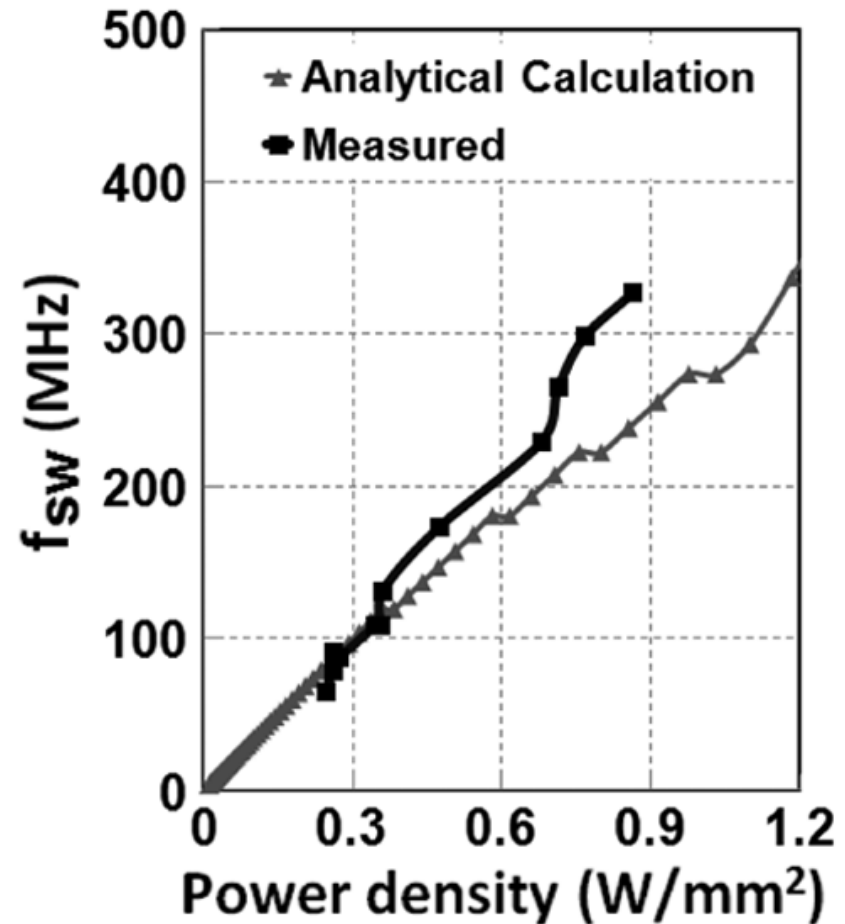 



- Measured with $n = 1/2$ ($V_i = 2V$, $V_o \approx 0.88V$)
- Matches analysis: $\sim 80\%$ efficiency @ 0.86 W/mm^2

Measured Efficiency vs. Topologies

 - All three topologies functional
 - (3:1 efficiency limited by breakdown)
- Efficiency still >70% for 0.75V – 1.15V V_o with 2V V_{in}





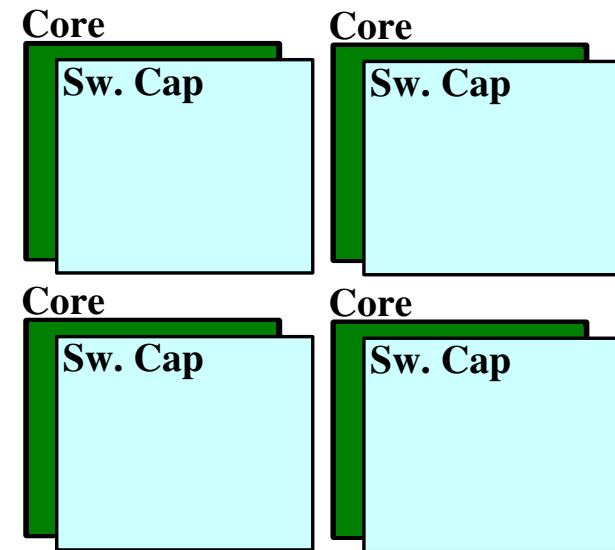 Looking Forward: Leveraging 2.5/3D Integration



- **Enables converter to use entire area over core**
 - Mitigates efficiency vs. power density tradeoff
- **Converter die can use older, lower-cost technology**
 - While still meeting efficiency & density requirements

Looking Forward: Dense Capacitors

  

- **Dense capacitors already exist for DRAM/eDRAM**
 - IBM eDRAM 2:1 converter*: 90% efficiency @ $2.3A/mm^2$
- **Opportunity to further leverage stacked DRAM**

*L. Chang *et al.*, "A Fully Integrated Switched-Capacitor 2:1 Voltage Converter with Regulation Capability and 90% Efficiency at $2.3A/mm^2$," *IEEE Symposium on VLSI Circuits*, Jun. 2010

Summary

- **Clear need for fully-integrated DC-DC converters**
 - Multiple off-chip supplies costly, degrade impedance
- **Switched-capacitor converters in standard CMOS can achieve:**
 - In 2:1: ~**80% efficiency @ 0.86 W/mm²**
 - **>70% efficiency** for **V_o from ~0.75V to 1.15V** with **V_i = 2V**
- **Low-cost technologies to enable even higher densities, efficiencies already exist**

Acknowledgments

- **BWRC students, faculty, and staff**

- **Focus Center Research Program**
 - IFC and C2S2

- **AMD**
 - Sam Naffziger, Vishvesh Sathe, Rich DeSantis

- **IBM Faculty Award**